

On the following pages, a description is given of the equations, structures and symbols for the adaptors that are referred to in the (L)WDF Toolbox, viz.

- the three-port series adaptor,
- the three-port parallel adaptor, and
- the two-port adaptor.

The reader is referred to the literature for the theory behind (Lattice) Wave Digital Filters. Especially noteworthy are the articles from Fettweiss and Gazsi:

A. Fettweis  
*Wave Digital Filters: Theory and Practice* (Invited Paper)  
Proc. of the IEEE, Vol. 74, No. 2, Februari 1986

L. Gazsi  
*Explicit Formulas for Lattice Wave Digital Filters*  
IEEE Trans. on CAS, Vol. 32, pp. 68-88, Jan 1985

Huibert J. Lincklaen Arriëns  
this version: January 2006

# 1 The Three-Port Series Adaptor

Given the equations directly following from Figure 1

$$U_1 + U_2 + U_3 = 0 \quad \text{and} \quad I_1 = I_2 = I_3 \quad (1)$$

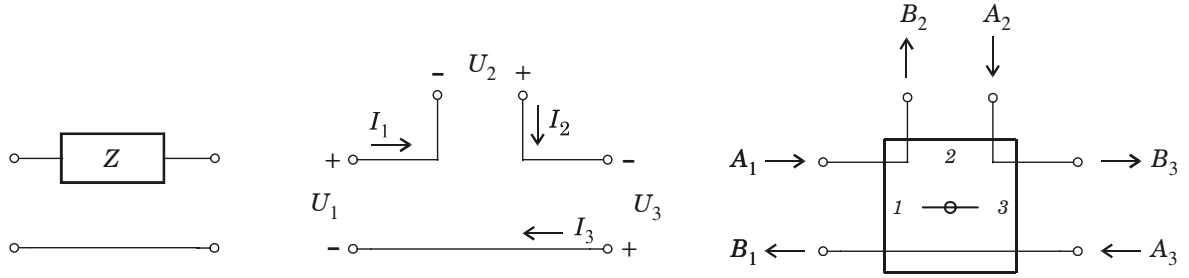


Figure 1: Definitions with respect to the three-port serial adaptor

and the definitions of the voltage wave variables

$$A_k = U_k + I_k R_k \quad (2a)$$

$$B_k = U_k - I_k R_k \quad (2b)$$

which can be rewritten as

$$U_k = \frac{A_k + B_k}{2} \quad \text{and} \quad I_k = \frac{A_k - B_k}{2R_k} \quad \text{with } k = 1, 2, 3 \quad (3)$$

we can perform the following derivations by combining equations (1) and (3)

$$A_1 + B_1 + A_2 + B_2 + A_3 + B_3 = 0 \quad (4)$$

$$\frac{A_1 - B_1}{R_1} = \frac{A_2 - B_2}{R_2} = \frac{A_3 - B_3}{R_3} \quad (5)$$

So, if we eliminate  $B_2$  and  $B_3$

$$B_2 = \frac{R_2}{R_1}(B_1 - A_1) - A_2 \quad \text{and} \quad B_3 = \frac{R_3}{R_1}(B_1 - A_1) - A_3 \quad (6)$$

we can express  $B_1$  in terms of the  $A$ -inputs

$$\left(1 + \frac{R_2}{R_1} + \frac{R_3}{R_1}\right) B_1 = \left(-1 + \frac{R_2}{R_1} + \frac{R_3}{R_1}\right) A_1 - 2A_2 - 2A_3$$

$$B_1 = \left(1 - \frac{2R_1}{R_1 + R_2 + R_3}\right) A_1 - \frac{2R_1}{R_1 + R_2 + R_3} A_2 - \frac{2R_1}{R_1 + R_2 + R_3} A_3 \quad (7)$$

If we define

$$\frac{2R_1}{R_1 + R_2 + R_3} = \alpha_1 \quad (8)$$

then (7) reduces to

$$B_1 = (1 - \alpha_1)A_1 - \alpha_1 A_2 - \alpha_1 A_3 \quad (9)$$

More generally

$$B_k = A_k - \alpha_k (A_1 + A_2 + A_3) \quad \text{where} \quad \alpha_k = \frac{2R_k}{R_1 + R_2 + R_3} \quad (10)$$

It also follows that

$$\alpha_1 + \alpha_2 + \alpha_3 = 2 \quad \text{while} \quad 0 \leq \alpha_k \leq 2 \quad (11)$$

We can write the wave equations in matrix notation:  $\mathbf{B} = \hat{\mathbf{S}} \cdot \mathbf{A}$

$$\begin{bmatrix} B_1 \\ B_2 \\ B_3 \end{bmatrix} = \begin{bmatrix} 1 - \alpha_1 & -\alpha_1 & -\alpha_1 \\ -\alpha_2 & 1 - \alpha_2 & -\alpha_2 \\ -\alpha_3 & -\alpha_3 & 1 - \alpha_3 \end{bmatrix} \cdot \begin{bmatrix} A_1 \\ A_2 \\ A_3 \end{bmatrix} \quad (12)$$

If we now eliminate  $\alpha_2$  by realizing (see equation (11)) that

$$\alpha_2 = 2 - \alpha_1 - \alpha_3 \quad (13)$$

we obtain for the matrix  $\hat{\mathbf{S}}$

$$\hat{\mathbf{S}} = \begin{bmatrix} 1 - \alpha_1 & -\alpha_1 & -\alpha_1 \\ \alpha_1 + \alpha_3 - 2 & \alpha_1 + \alpha_3 - 1 & \alpha_1 + \alpha_3 - 2 \\ -\alpha_3 & -\alpha_3 & 1 - \alpha_3 \end{bmatrix} \quad (14)$$

Such an adaptor can be denoted as a Three-Port Series adaptor with Port 2 being *dependent*, more generally called an *unconstrained* three-port series adaptor.

A possible realization using 2 (constant coefficient) multipliers, 4 adders and 1 sign-inverter is given in Figure 2. The seriesl adaptor can be used to connect a single component in a series arm of a ladder structure, but also to connect the (translated) inductor and capacitor of a series resonator. A component determines the  $R$ -value of its port, while all three  $R$ -values are needed to obtain the multiplier constants  $\alpha_1$  and  $\alpha_3$ .

Now if, e.g. in a ladder structure, we connect two adaptors (suppose Port 3 of this adaptor to Port 1 of a next one), we can freely choose the resistance value for these ports.

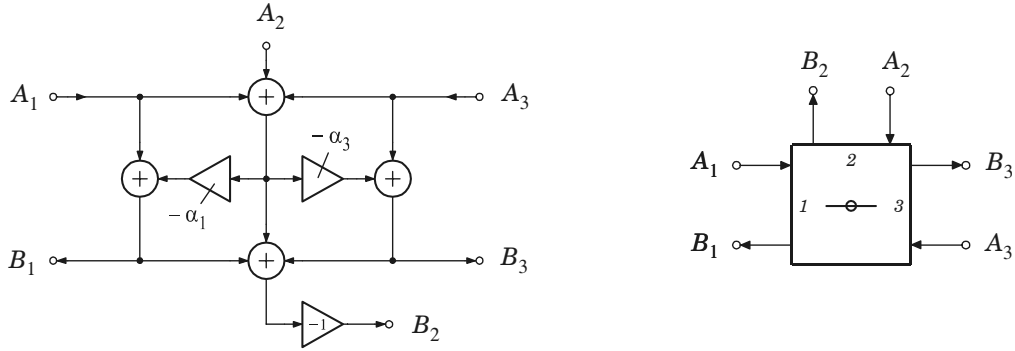


Figure 2: Signal-flow diagram for realizing the  $\hat{S}$ -matrix of Equation 14 and its commonly used symbol.

Suppose, we choose for the first adaptor

$$R_3 = R_1 + R_2 \quad (15)$$

then we get

$$\alpha_3 = 1 \quad (16)$$

and we find that  $B_3$  becomes independent of  $A_3$ , as can be seen from

$$\hat{S} = \begin{bmatrix} 1 - \alpha_1 & -\alpha_1 & -\alpha_1 \\ \alpha_1 - 1 & \alpha_1 & \alpha_1 - 1 \\ -1 & -1 & 0 \end{bmatrix} \quad (17)$$

In this case, we obtain a Three-Port Series adaptor with *reflection-free* Port 3 and Port 2 being dependent, which can be indicated as a *constrained* three-port series adaptor.

Figure 3 shows a possible realization and its commonly used symbol.


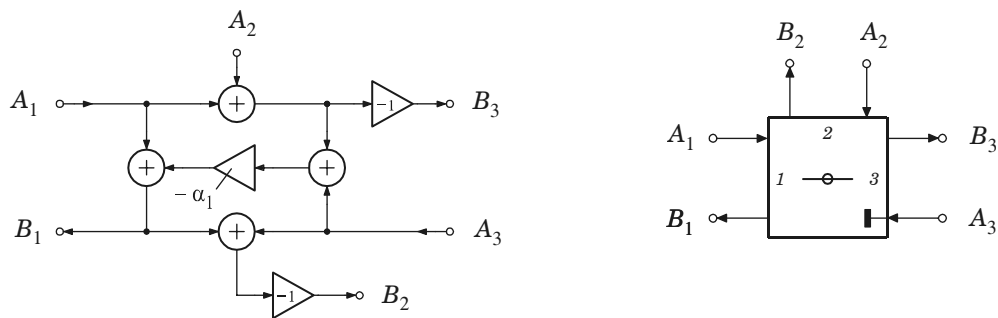


Figure 3: Possible structure for realizing the  $\hat{S}$ -matrix of Equation 17 and the symbol to represents it with.

## 2 The Three-Port Parallel Adaptor

Given the equations directly following from Figure 4

$$U_1 = U_2 = U_3 \quad \text{en} \quad I_1 + I_2 + I_3 = 0 \quad (18)$$

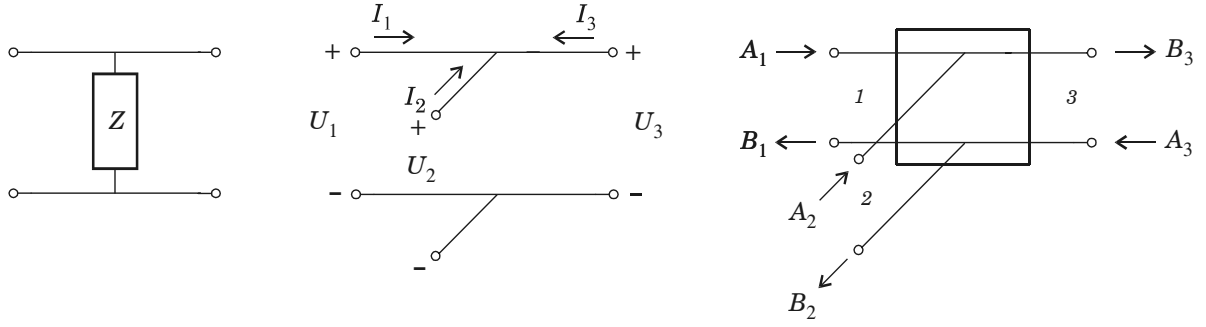

**Figure 4: Definitions with respect to the three-port parallel adaptor**

and the definitions of the voltage wave variables

$$A_k = U_k + I_k R_k \quad (19a)$$

$$B_k = U_k - I_k R_k \quad (19b)$$

we find

$$U_k = \frac{A_k + B_k}{2} \quad \text{and} \quad I_k = \frac{A_k - B_k}{2R_k} \quad \text{with } k = 1, 2, 3 \quad (20)$$

While  $g_k = \frac{1}{R_k}$ , we can perform the following derivations by combining equations (18) and (20)

$$g_1 (A_1 - B_1) + g_2 (A_2 - B_2) + g_3 (A_3 - B_3) = 0 \quad (21)$$

$$A_1 + B_1 = A_2 + B_2 = A_3 + B_3 \quad (22)$$

So, if we eliminate  $B_2$  and  $B_3$

$$B_2 = A_1 + B_1 - A_2 \quad \text{and} \quad B_3 = A_1 + B_1 - A_3 \quad (23)$$

we can express  $B_1$  in terms of the  $A$ -inputs

$$B_1 = \frac{g_1 - g_2 - g_3}{g_1 + g_2 + g_3} A_1 + \frac{2g_2}{g_1 + g_2 + g_3} A_2 + \frac{2g_3}{g_1 + g_2 + g_3} A_3 \quad (24)$$

If we define

$$\alpha_k = \frac{2g_k}{g_1 + g_2 + g_3} \quad (25)$$

then (24) reduces to

$$B_1 = (\alpha_1 - 1) A_1 + \alpha_2 A_2 + \alpha_3 A_3 \quad (26)$$

More generally

$$B_k = \alpha_1 A_1 + \alpha_2 A_2 + \alpha_3 A_3 - A_k \quad \text{where} \quad \alpha_k = \frac{2g_k}{g_1 + g_2 + g_3} \quad (27)$$

It also follows that

$$\alpha_1 + \alpha_2 + \alpha_3 = 2 \quad \text{while} \quad 0 \leq \alpha_k \leq 2 \quad (28)$$

We can write the wave equations in matrix notation:  $\mathbf{B} = \hat{\mathbf{S}} \cdot \mathbf{A}$

$$\begin{bmatrix} B_1 \\ B_2 \\ B_3 \end{bmatrix} = \begin{bmatrix} \alpha_1 - 1 & \alpha_2 & \alpha_3 \\ \alpha_1 & \alpha_2 - 1 & \alpha_3 \\ \alpha_1 & \alpha_2 & \alpha_3 - 1 \end{bmatrix} \cdot \begin{bmatrix} A_1 \\ A_2 \\ A_3 \end{bmatrix} \quad (29)$$

If we now eliminate  $\alpha_2$  by realizing (see equation (28)) that

$$\alpha_2 = 2 - \alpha_1 - \alpha_3 \quad (30)$$

we obtain for the matrix  $\hat{\mathbf{S}}$

$$\hat{\mathbf{S}} = \begin{bmatrix} \alpha_1 - 1 & 2 - \alpha_1 - \alpha_3 & \alpha_3 \\ \alpha_1 & 1 - \alpha_1 - \alpha_3 & \alpha_3 \\ \alpha_1 & 2 - \alpha_1 - \alpha_3 & \alpha_3 - 1 \end{bmatrix} \quad (31)$$

Such an adaptor can be denoted as a Three-Port Parallel adaptor with Port 2 being *dependent*, more generally called an *unconstrained* three-port parallel adaptor.

A possible realization using 2 (constant coefficient) multipliers, 4 adders and two sign-inversions is given in Figure 5. The parallel adaptor can be used to connect a single component in a shunt arm of a ladder structure, but also to connect the (translated) inductor and capacitor of a parallel resonator. A component determines the  $g$ -value of its port, while all three  $g$ -values are needed to obtain the multiplier constants  $\alpha_1$  and  $\alpha_3$ .

Now if, e.g. in a ladder structure, we connect two adaptors (suppose Port 3 of this adaptor to Port 1 of a next one), we can freely choose the resistance value for these ports.

Suppose, we choose for the first adaptor

$$g_3 = g_1 + g_2 \quad (32)$$

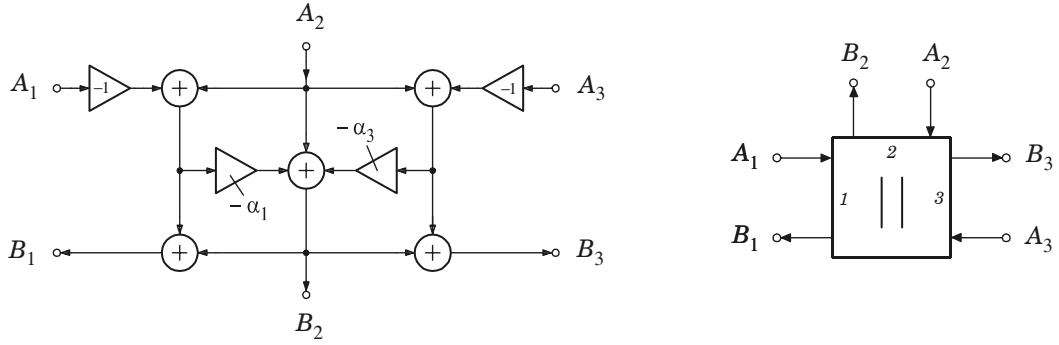


Figure 5: Possible structure for realizing the  $\hat{S}$ -matrix of Equation 31 and its commonly used symbol.

then we get

$$\alpha_3 = 1 \tag{33}$$

and we find that  $B_3$  becomes independent of  $A_3$ , as can be seen from

$$\hat{S} = \begin{bmatrix} \alpha_1 - 1 & 1 - \alpha_1 & 1 \\ \alpha_1 & -\alpha_1 & 1 \\ \alpha_1 & 1 - \alpha_1 & 0 \end{bmatrix} \tag{34}$$

In this case, we obtain a Three-Port Parallel adaptor with *reflection-free* Port 3 and Port 2 being dependent, which can be indicated as a *constrained* three-port parallel adaptor.

Figure 6 shows a possible realization and its commonly used symbol.

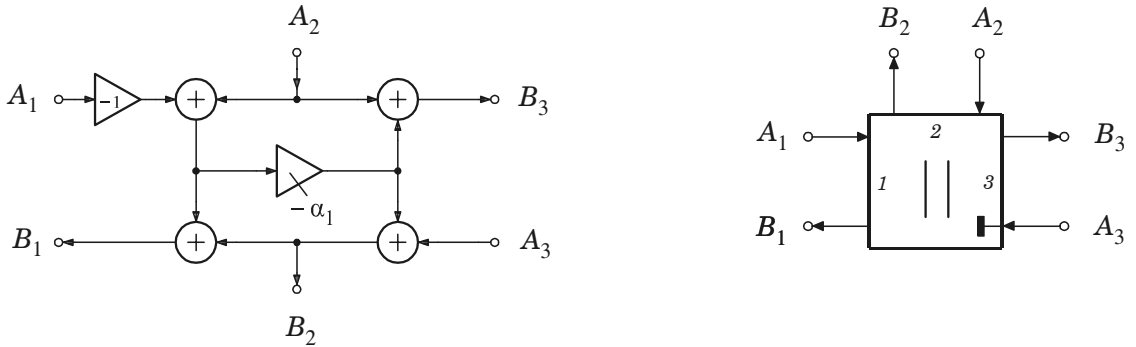


Figure 6: Possible structure for realizing the  $\hat{S}$ -matrix of Equation 34 and the symbol to represents it with.

### 3 The Two-Port Adaptor

Given the equations directly following from Figure 7

$$U_1 = U_2 \quad \text{and} \quad I_1 + I_2 = 0 \quad (35)$$

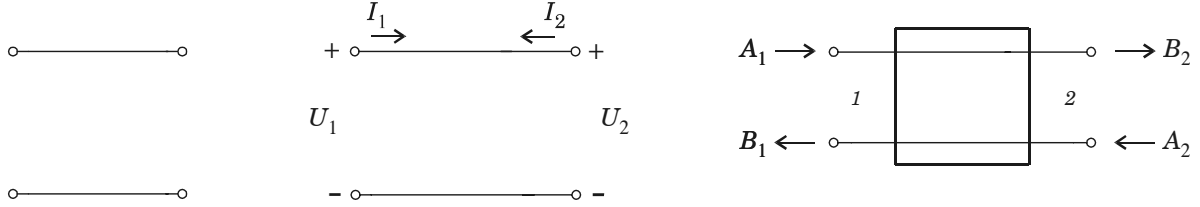


Figure 7: Definitions with respect to the two-port (parallel) adaptor.

and the definitions of the voltage wave variables

$$A_k = U_k + I_k R_k \quad (36a)$$

$$B_k = U_k - I_k R_k \quad (36b)$$

we find

$$U_k = \frac{A_k + B_k}{2} \quad \text{and} \quad I_k = \frac{A_k - B_k}{2R_k} = 2g_k (A_k - B_k) \quad \text{with } k = 1, 2 \quad (37)$$

While  $g_k = \frac{1}{R_k}$ , we can perform the following derivations by combining equations (35) and (37)

$$g_1 (A_1 - B_1) + g_2 (A_2 - B_2) = 0 \quad (38)$$

$$A_1 + B_1 = A_2 + B_2 \quad (39)$$

So, if we eliminate  $B_2$

$$-B_2 = -A_1 - B_1 + A_2 \quad (40)$$

we can express  $B_1$  in terms of the  $A$ -inputs

$$B_1 = \frac{g_1 - g_2}{g_1 + g_2} A_1 + \frac{2g_2}{g_1 + g_2} A_2 \quad (41)$$

If we define

$$\alpha_k = \frac{2g_k}{g_1 + g_2}$$



then (24) reduces to

$$B_1 = (\alpha_1 - 1) A_1 + \alpha_2 A_2 \quad (42)$$

More generally

$$B_k = \alpha_1 A_1 + \alpha_2 A_2 - A_k \quad (43)$$

It also follows that

$$\alpha_1 + \alpha_2 = 2 \quad \text{while} \quad 0 \leq \alpha_k \leq 2 \quad (44)$$

We can write the wave equations in matrix notation:  $\mathbf{B} = \hat{\mathbf{S}} \cdot \mathbf{A}$

$$\begin{bmatrix} B_1 \\ B_2 \end{bmatrix} = \begin{bmatrix} \alpha_1 - 1 & \alpha_2 \\ \alpha_1 & \alpha_2 - 1 \end{bmatrix} \cdot \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} \quad (45)$$

If we now eliminate  $\alpha_2$  by realizing (see equation (44) ) that

$$\alpha_2 = 2 - \alpha_1$$

we obtain for the matrix  $\hat{\mathbf{S}}$

$$\hat{\mathbf{S}} = \begin{bmatrix} \alpha_1 - 1 & 2 - \alpha_1 \\ \alpha_1 & 1 - \alpha_1 \end{bmatrix} \quad (46)$$

Such an adaptor can be denoted as a Two-Port adaptor. A possible realization using only one (constant coefficient) multiplier, 3 adders and one sign-inversion is given in Figure 8a.

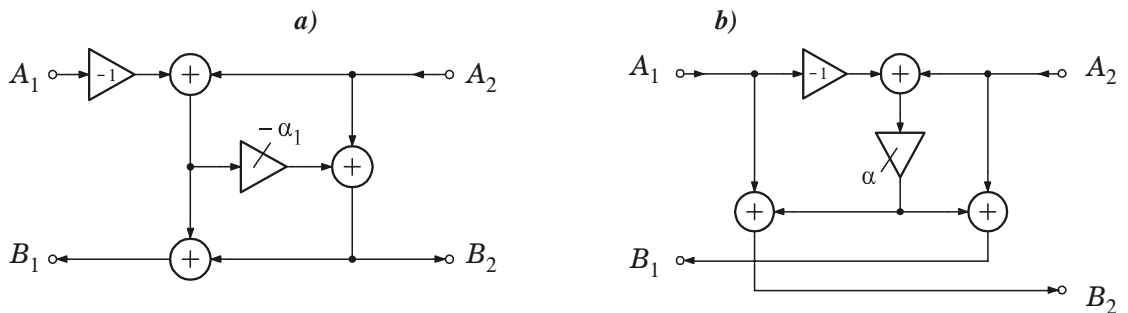


Figure 8: Possible structures for realizing a) the  $\hat{\mathbf{S}}$ -matrix of Equation 46, and b) the  $\hat{\mathbf{S}}$ -matrix of Equation 48.

We can introduce a new variable  $\alpha$ , with  $\alpha = 1 - \alpha_1$ , for which can be derived that


$$\alpha = \frac{R_1 - R_2}{R_1 + R_2} \quad (47)$$

to find an alternative  $\hat{\mathbf{S}}$  matrix:

$$\hat{\mathbf{S}} = \begin{bmatrix} -\alpha & 1 + \alpha \\ 1 - \alpha & \alpha \end{bmatrix} \quad (48)$$

with a possible realization shown in Figure 8b.

Figure 9 shows two symbols to identify a two-port with. Figure 9a is the most widely used, but we prefer to use the simple version of 9b in our MATLAB drawings.

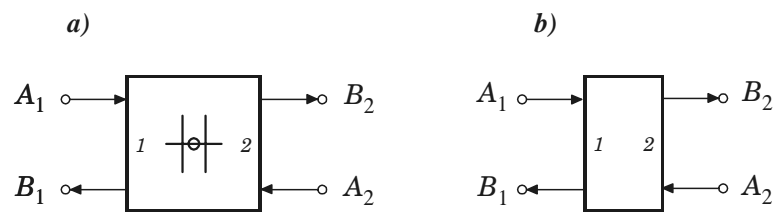

**Figure 9: Two symbols to be used for a two-port adaptor in block diagrams.**